

# **Digital Logic Design (EL-1005)**

## **LABORATORY MANUAL**

### **Spring-2022**



## **LAB 08**

### **Binary Comparator**

---

STUDENT NAME

---

ROLL NO

---

SEC

---

INSTRUCTOR SIGNATURE& DATE

**MARKS AWARDED: /10**

---

NATIONAL UNIVERSITY OF COMPUTER AND EMERGING SCIENCES (NUCES), KARACHI

---

## Lab Session 08: Binary Comparator

---

### **OBJECTIVES:**

- To learn and understand how to design a multiple output combinational circuit
- To learn and understand the working of 2-bit binary comparator
- To learn and understand the working and usage of Exclusive-OR and Exclusive-NOR gates

**APPARATUS:** Logic trainer, Logic probe

**COMPONENTS:** ICs 74LS08, 74LS32, 74LS04, 74LS86, 74LS02

### **THEORY:**

Binary comparator is a combinational circuit that compares magnitude of two binary data signals A & B and generates the results of comparison in the form of three output signals  $A > B$ ,  $A = B$ ,  $A < B$ . Binary comparator is a multiple input and multiple output combinational circuit. When a combinational circuit has two or more than two outputs then each output is expressed separately as a function of all inputs. Separate K-map is made for each output.

### **One-bit comparator:**

One-bit comparator compares magnitude of two numbers A and B, 1 bit each, and generates the comparison result. The result consists of three outputs let us say L, E, G, so that

$$L = 1 \text{ if } A < B$$

$$E = 1 \text{ if } A = B$$

$$G = 1 \text{ if } A > B$$

### **Truth Table:**

Inputs		Outputs		
A	B	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

### K-Maps for Outputs:

A \ B	0	1
0		1
1		

K-Map for Output L

A \ B	0	1
0	1	
1		1

K-Map for Output E

A \ B	0	1
0		
1	1	

K-Map for Output G

### Boolean Expressions of Outputs:


L:  $\bar{A}B$

E:  $AB + \bar{A}\bar{B}$

G:  $A\bar{B}$
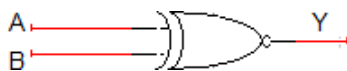
### Exclusive-OR & Exclusive-NOR gates:

The figure given below shows the symbol of Exclusive-OR (XOR) and Exclusive-NOR (XNOR) gates.




XNOR gate




XOR gate

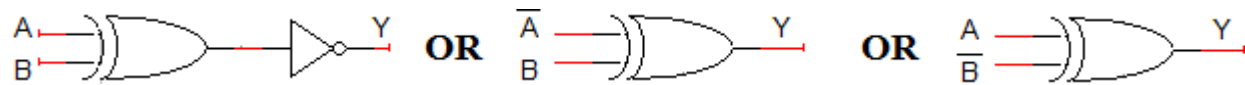Boolean expression of XNOR gate is  $AB + \bar{A}\bar{B}$  and Boolean expression of XOR is  $\bar{A}B + A\bar{B}$ . Boolean expression of XNOR gate can be implemented using XOR gate as shown in figure below:


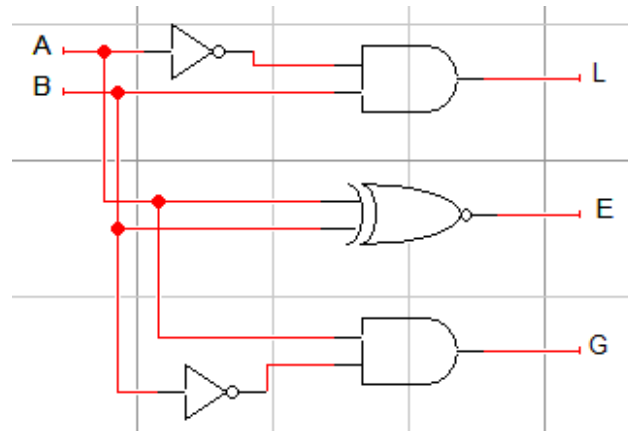
### Circuit Diagram for one-bit comparator:




In this experiment 74LS86 IC will be used for implementation of XOR gate function. 74LS86 IC contains four 2-input XOR gates. The function table and connection diagram for this IC are shown below:

### Function Table:

Inputs		Output
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

H= Logic High, L= Logic Low

### Connection Diagram:

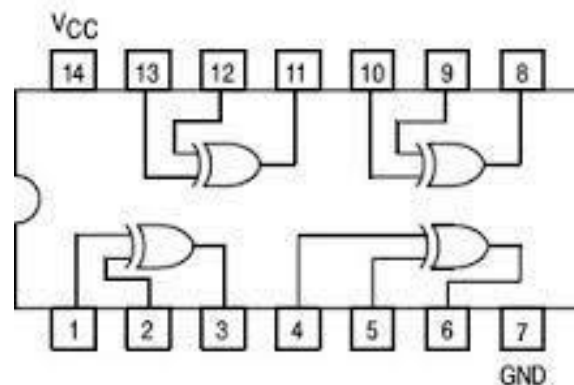

**Lab Task #1**

Design a combinational circuit that compares two 2-bit numbers and generates the comparison result. The result consists of three outputs let us say L, E, G, so that

$$L = 1 \text{ if } A < B$$

$$E = 1 \text{ if } A = B$$

$$G = 1 \text{ if } A > B$$

1. Write truth table

### **Lab Task #2**

2. Find minimal SOP expressions for the outputs L, E, and G using K-map. Draw separate K-map for each output in the space given below

### **Lab Task #3**

Implement the combinational circuit of 2-Bit Binary comparator on Logisim/Logic Works.

### **Lab Task #4**

Design Full Adder IC in Logic Works

### **INSTRUCTION FOR SUBMISSION**

Upload circuits of Task # 3 on Google Classroom